

**2024A9**
**CIRCUITS, RESISTANCE**

Level 1: Figure 4:

$$\frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)$$


$$\frac{1}{R_{eq}} = \left( \frac{1}{150\Omega} + \frac{1}{60\Omega} + \frac{1}{200\Omega} \right)$$

$$\frac{1}{R_{eq}} = 0.02833\Omega$$

$$R_{eq} = \frac{1}{0.02833\Omega}$$

$$R_{eq} = 35.3\Omega$$

Level 2:

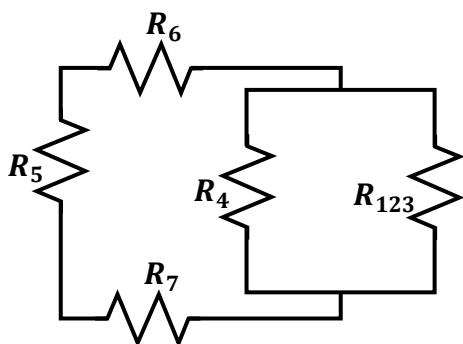

$$R_{12} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$R_{12} = \left( \frac{1}{200\Omega} + \frac{1}{350\Omega} \right)^{-1}$$

$$R_{12} = 127.27\Omega$$

$$R_{123} = R_{12} + R_3$$




$$R_{123} = 127.27\Omega + 50\Omega$$

$$R_{123} = 177.27\Omega$$

$$R_{1234} = \left( \frac{1}{R_{123}} + \frac{1}{R_4} \right)^{-1}$$

$$R_{1234} = \left( \frac{1}{177.27\Omega} + \frac{1}{500\Omega} \right)^{-1}$$

$$R_{1234} = 130.87\Omega$$

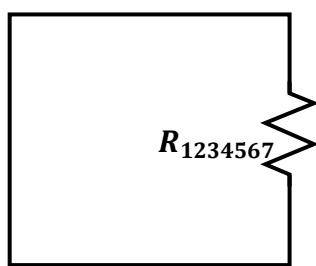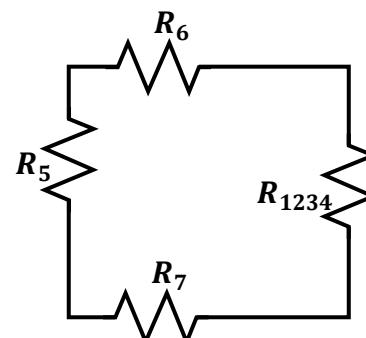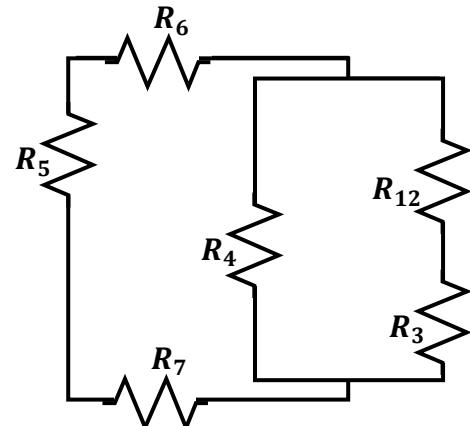

$$R_{1234567} = R_{1234} + R_5 + R_6 + R_7$$

$$R_{1234567} = 130.87\Omega + 180\Omega + 100\Omega + 220\Omega$$

$$R_{1234567} = 630.87\Omega$$

$$R_{eq} = R_{1234567} = 630.87\Omega$$